

Assignment:- 7.

Date _____
Page _____


D/A and A/D converters:-

(1) Explain D/A converter R-2R ladder circuit.

→ A digital to analog converter converts a digital input signal into an analog output signal.

→ The Digital signal is represented with a binary code, which is combination of bits 0 and 1.

→ Block diagram:-

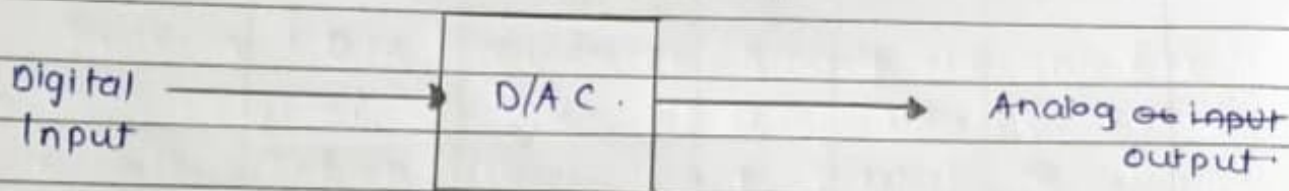

→ R-2R ladder circuit:-


→ R-2R ladder is removed the disadvantage of binary weighted resistor to design more accurate resistor.

→ R-2R ladder produces an analog output which is almost equal to digital input signal by using ladder.

→ The R-2R ladder network uses just two resistor value. R and 2R.

Date _____
Page _____

→ Circuit diagram of 3-bit R-2R ladder:

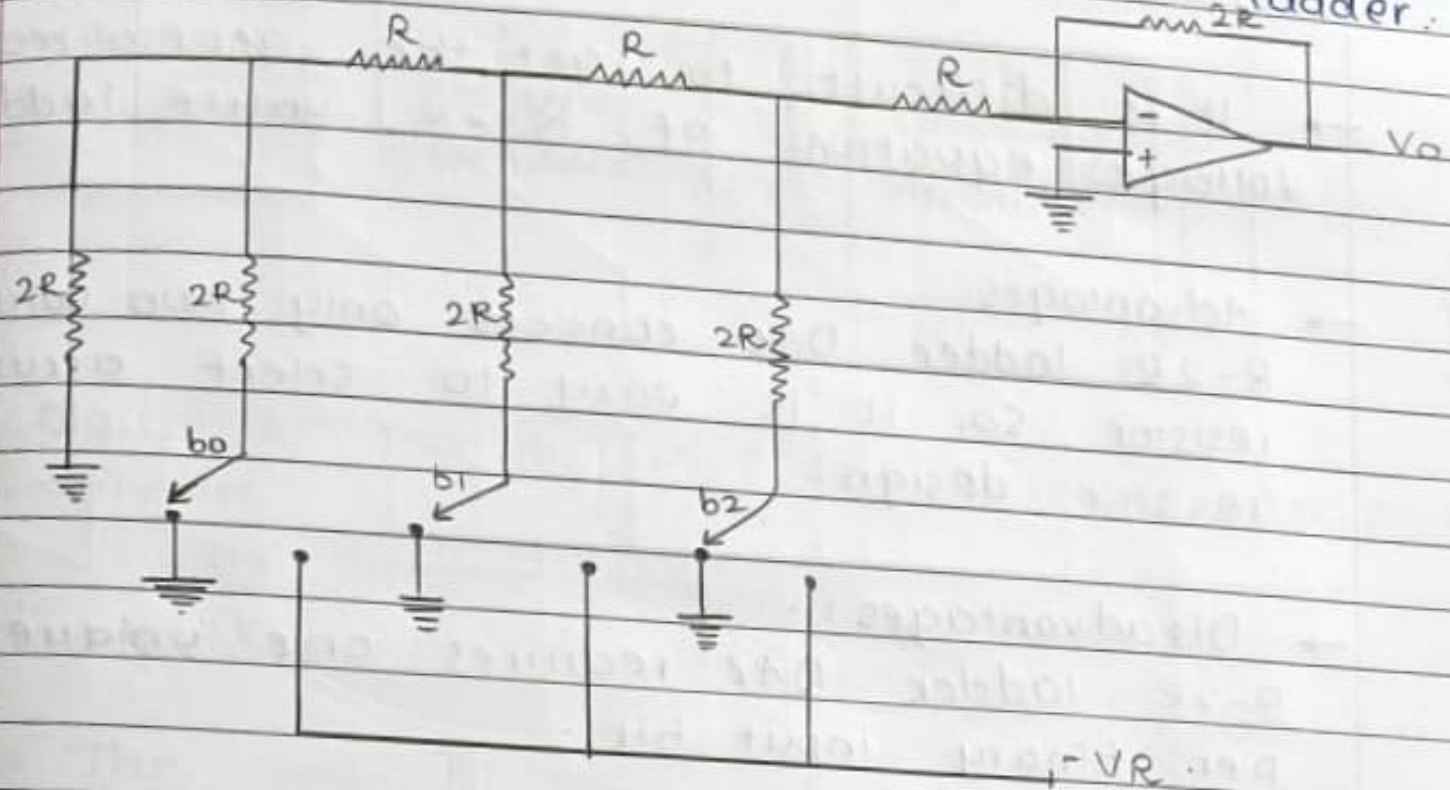

- This is a 3-bit binary input R-2R ladder so input is b_2 , b_1 , and b_0 .
- In this circuit diagram, b_2 input is denoted by most significant bit.
- b_0 input is denoted by least significant bit.
- In this ckt, Digital switch are connected to ground, then corresponding to ground input bits are equal to '0'.
- In this ckt, Digital switch are connected to the negative reference voltage $-V_R$ the

corresponding input bits are equal to '1'.

→ It is difficult to get the generalized output voltage equation of R-2R ladder.

→ Advantages:-

R-2R ladder DAC consists only two values of resistor so, it is easy to select accurate resistor design.

→ Disadvantages:-

R-2R ladder DAC requires one unique value per binary input bit.


(2) Explain DIA converter binary weighted resistor.

→ A weighted resistor DAC produces an analog output, which is almost equal to digital input signal by using binary weighted resistor.

→ Binary weighted Resistor is a type of Data converter which converts a digital binary number into a equivalent analog output number.

→ Block Diagram:-

→

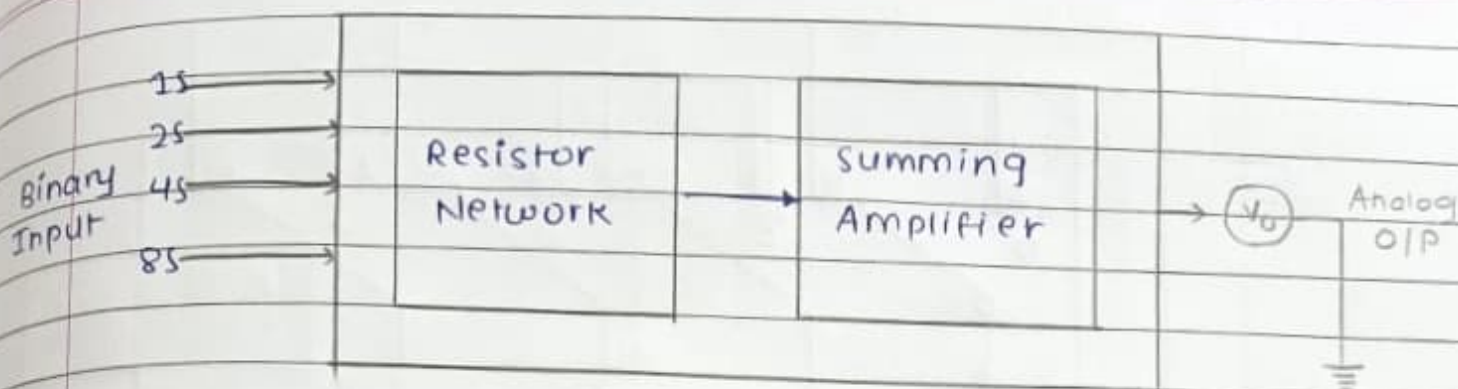


Digital to Analog Converter's converts into two circuits.

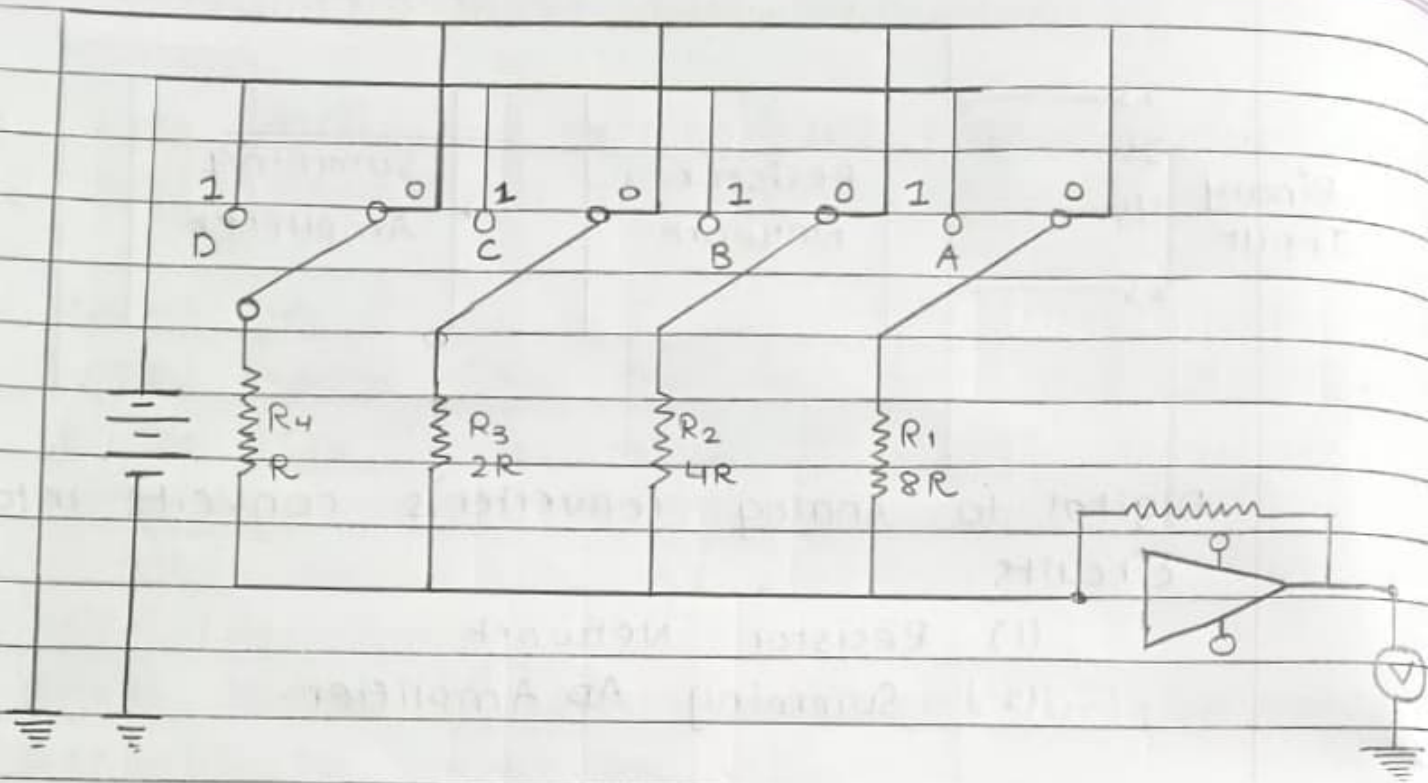- (1) Resistor Network
- (2) Summing ~~AP~~ Amplifier.

- The analog output voltage is monitored with a voltmeter.
- In Resistor Network most lowest resistor value is called most significant Bit.
- In Resistor Network most highest resistor value is called least significant Bit.
- Circuit Diagram :-





- In this ckt diagram, Most lowest Resistor value is R_4 , so, R_4 is a most significant bit in the resistor network.
- Most highest value is R_1 . So, R_1 is a least significant bit in the Resistor network.
- When all the Bit are high in the ckt then,

$$\text{Current for A Bit } I_0 = \frac{V_{in}}{8R}$$

$$\text{Current for B Bit } I_1 = \frac{V_{in}}{4R}$$

$$\text{Current for C Bit } I_2 = \frac{V_{in}}{2R}$$

current for 0 Bit $I_3 = \frac{V_{in}}{R}$

Total current in the ckt,

$$I = I_0 + I_1 + I_2 + I_3$$

$$= \frac{V_{in}}{8R} + \frac{V_{in}}{4R} + \frac{V_{in}}{2R} + \frac{V_{in}}{R}$$

$$= \frac{V_{in}}{R} (0.125 + 0.25 + 0.5 + 1)$$

$$= I = 1.875 \frac{V_{in}}{R}$$

→ When Bit are low in the ckt then,
Total current $I = 0$.

→ Advantages: Binary weighted Resistor is simple in construction and provides fast conversion.


→ Disadvantages:- It is difficult to design more accurate resistor in the resistor Network.

(3) Explain counter type A/D converter.

→ A counter type ADC produces a digital output which is approximately equal to analog input.

→ A counter type ADC produces a digital output using comparator and counter operation.

→ Block Diagram.

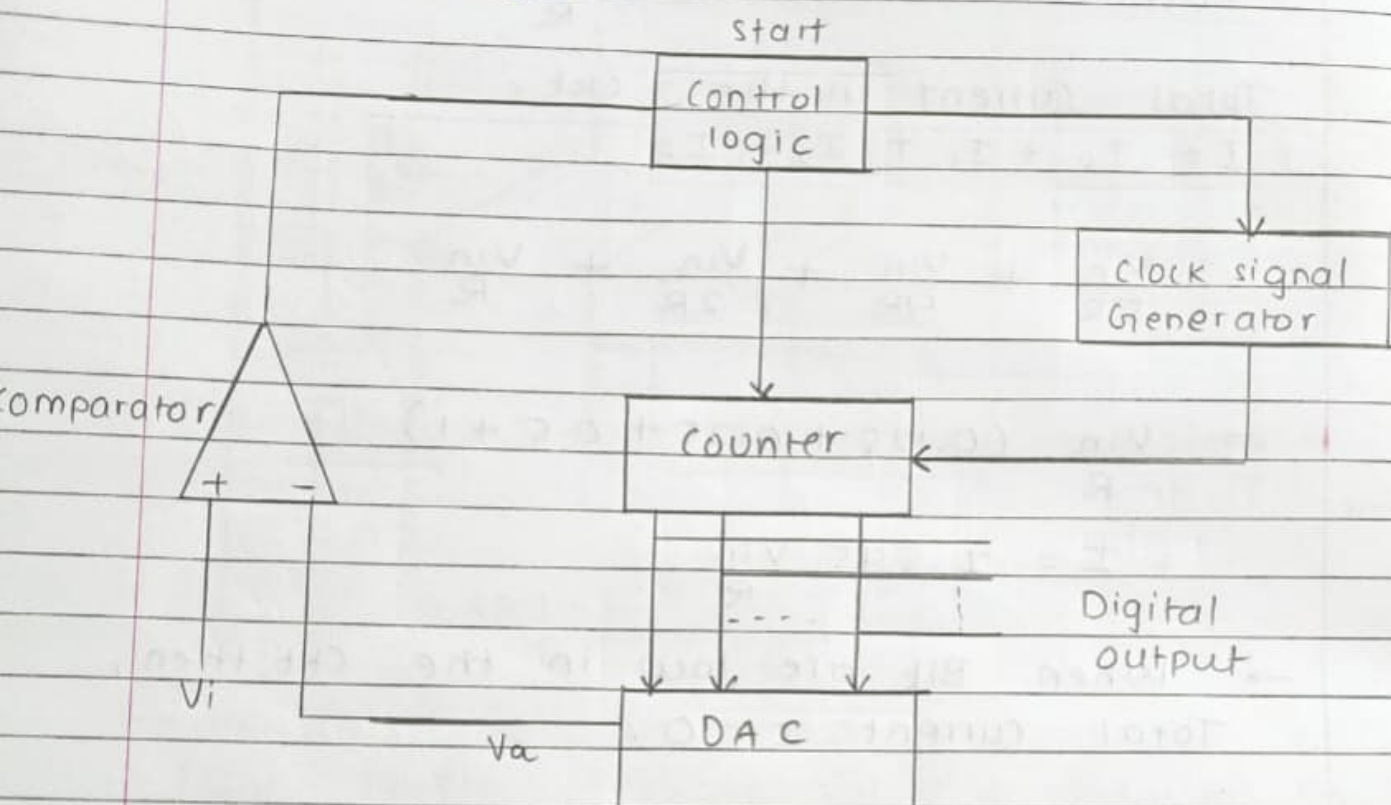

→ This counter type ADC consist comparator, counter, control logic, clock signal generator and DAC

→ Working:


The control logic reset the counter and enables to clock signal and send a clock pulse to the counter.

→ Counter gets incremented by every clock pulse and its binary format output applied as an input of DAC.

- DAC converts the received binary input into the analog output.
 - Comparator compares the analog value V_a with external analog input V_i .
 - If $V_i > V_a$, then output comparator will generate '1'.
 - If $V_i \leq V_a$, then output comparator will generate '0'.
 - And control logic send the clock pulse to the counter and counter will display the digital output.
- (4) Explain Successive Approximation A/D converter.
- A successive Approximation ADC produces a digital output which is approximately equal to analog input.
 - A successive Approximation ADC produces a digital output using successive approximation method.

→

→ Block Diagram:-

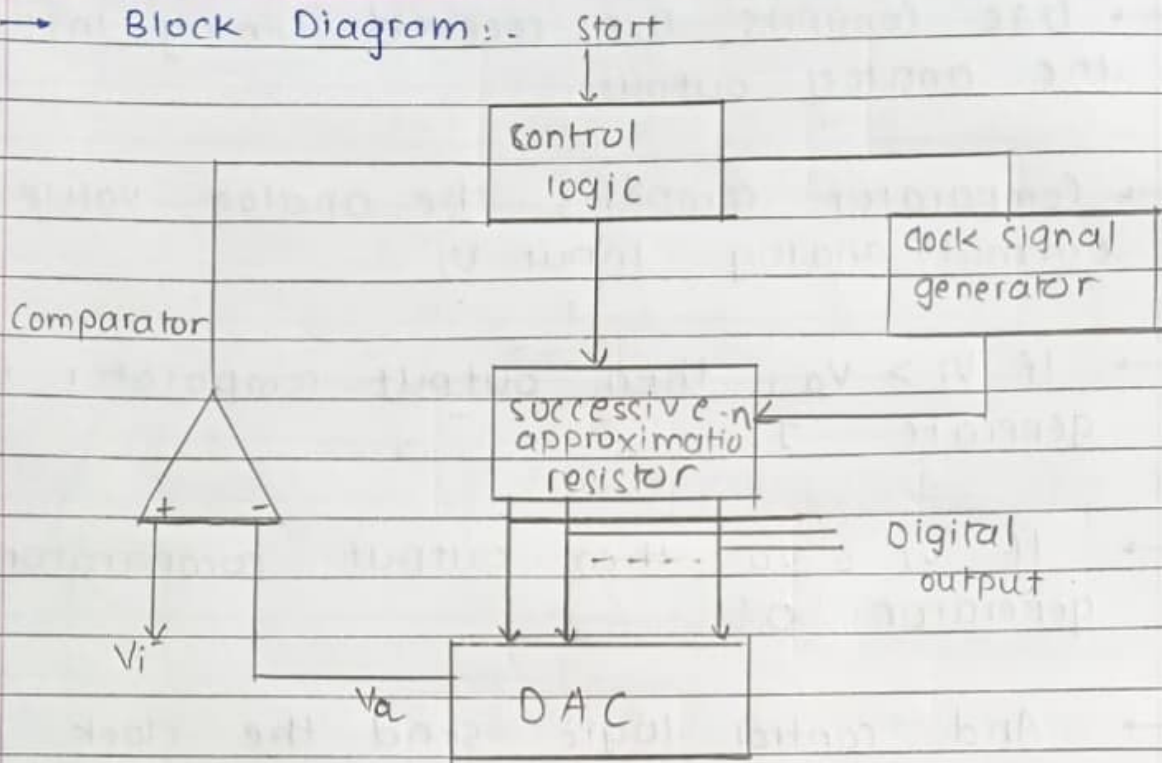

→ This Successive Approximation ADC consist comparator, Control logic, clock signal generator, Successive Approximation Resistor and DAC.

→ Working:-

Control logic reset the Successive approximation resistor and enable to clock signal to send a clock pulse to the Successive resistor.

→ Successive Approximation Resistor update clock pulse and binary format output applied as a input of DAC.

→ DAC converts the received binary input into the analog output.

→ Comparator compares the analog value V_a with external analog value V_i .

→ If $V_i > V_a$ then output comparator generates '1'.

→ If $V_i \leq V_a$, then output comparator generates '0'.

→ After that control logic send SAR with clock pulse and SAR display the digital output.


(5) Explain Dual slope type A/D converter.

→ A Dual slope ADC produces an equivalent digital output for a corresponding analog input.

→ A Dual slope ADC produces an digital output using Dual slope Technique.



Block Diagram:

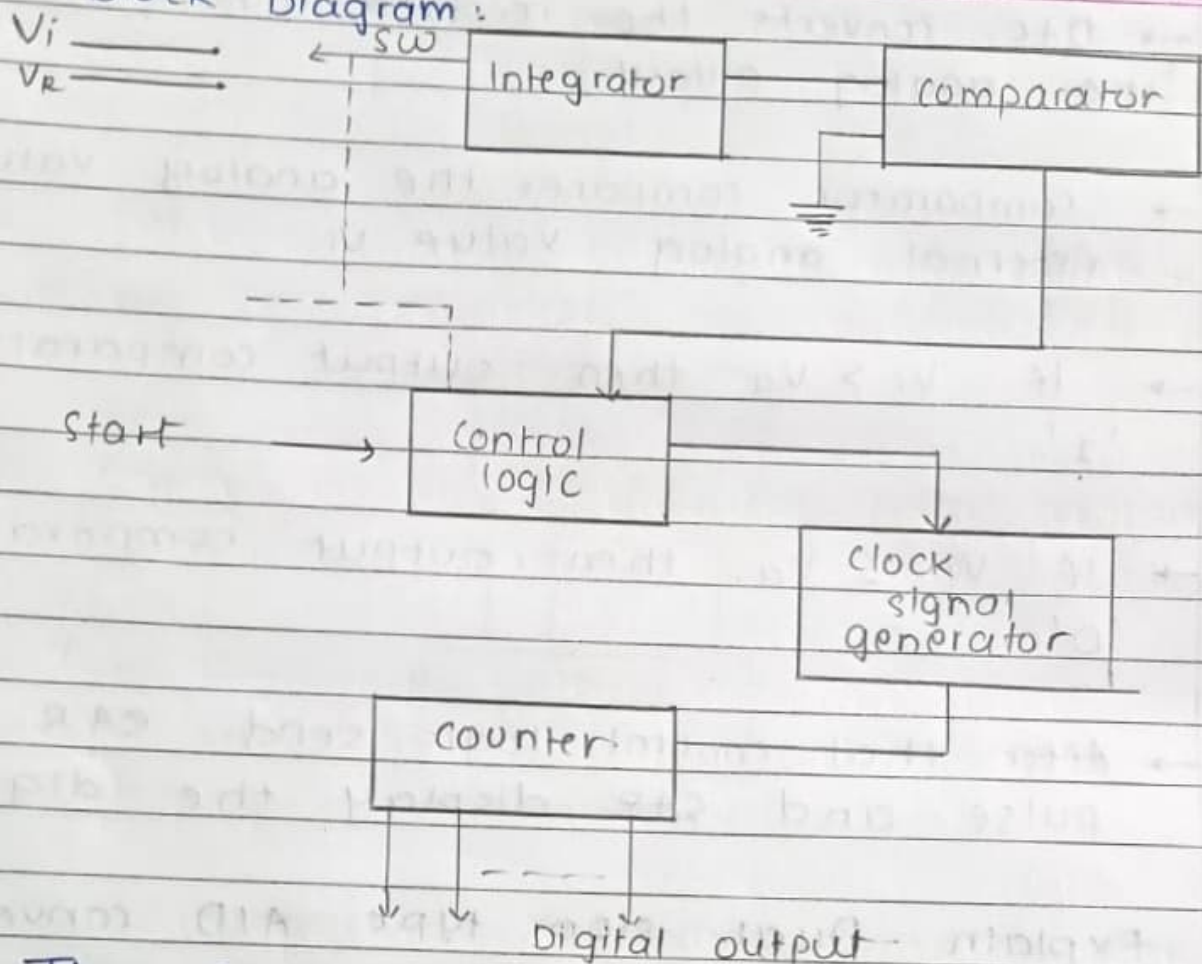

→ The Dual slope ADC consist Integrator, Comparator, clock signal generator, Control logic and counter.

→ Working:

→ Control logic pushes the switch SW to connect the external voltage V_i , when it received the start signal.

→ The input voltage is applied to Integrator.

→ The output of integrator is connected to the comparator input and second input of comparator connect with ground.

- comparator compares the integrator output and ground input and produces output to applied the control logic.
- The counter get increment by clock pulse and control logic push switch sw to connect negative reference voltage.
- The negative reference voltage applied to integrator and remove charge until it become zero.
- The output of integrator become input of comparator and comparator compare the both input having zero volts.
- So, comparator send a signal to control logic. Control logic disable to clock signal and holds counter value.
- The counter value is display output as a digital signal.

1) Explain D/A converter specifications.

- A digital-to-analog (D/A) converter (DAC) is an essential component in electronics, converting digital signals into analog signals.

→ Understanding its specifications is important for selecting the right DAC for specific applications.

→ (1) Resolution: Refers to the number of bits the DAC uses to represent an analog output.

→ Higher resolution provides finer granularity in the output signal.

→ (2) Sampling Rate: Specifies how fast the DAC can convert digital data into analog signals.

→ Usually measured in samples per second, it determines the maximum frequency of the signal that the DAC can output accurately.

→ (3) Output Range:- The range of analog voltages or currents that the DAC can produce.

→ For example, a DAC with a 0 to 5V output range can generate signals between 0 and 5 volts.

(4) Linearity :- Describes how accurately the output analog signal matches the ideal straight-line response.

- (5) Monotonicity: Ensures that the DAC output either increases or stays the same as the digital input increases, without ever decreasing.
 - (6) Settling Time: The time it takes for the DAC output to stabilize within a specified error band after a digital input code is applied.
 - (7) Glitch energy: Refers to unwanted signal transients that occur when the DAC switches between output levels, especially during significant code changes.
 - Lower glitch energy is preferable for smooth signal output.
- 7) Explain the A/D converter specifications.
- An analog-to-digital (A/D) converter (ADC) converts analog signals into digital signals.
 - The performance of an ADC is critical in systems like data acquisition, signal processing, and communication systems.
 - The number of bits used to represent the analog signal in digital form is known as resolution.
 - Higher resolution is needed in applications requiring precise measurements.

- The no. of samples the ADC can take per second, usually measured in samples per second (SPS) or Hertz (Hz).
- High sampling rates are needed for high-frequency signals, such as in radar systems or digital communication.
- The range of analog voltages that the ADC can convert to digital values.
- Suitable for applications where the signal's amplitude varies greatly.
- The ratio between the magnitude of the signal and the background noise.
- Important in high-precision audio or instrumentation applications.
- The actual resolution of the ADC when considering noise and other non-idealities.
- Important in high-precision applications, where actual performance matters more than theoretical resolution.

(8) Explain Flash Type A/D converter.

- A Flash type ADC produces an equivalent digital output for a corresponding analog input.
- A Flash type ADC produces a digital output using priority encoder.
- This is a 3-bit Flash type ADC circuit diagram.
- The 3-bit Flash type ADC consists of a voltage divider network, 7 comparators and a priority encoder.
- working: The voltage divider network contains 8 equal resistors. V_R voltage is applied to the entire network.
- The external input voltage V_i is applied to the non-inverting terminal of comparators.
- At a time, all the comparators compare the external input with reference voltage.
- If $V_i >$ voltage drop, then output comparator will generate '1'.
- If $V_i <$ voltage drop, then output comparator will generate '0'.

→ All the outputs of comparators are connected as the input of priority encoder.

→ This Priority encoder produces a binary output.

