

LDRP-ITR, Gandhinagar/VSITR, KADI

Semester: 3 (CE/IT/CSE) All division

Subject Name: Digital Electronics

Assignment-7

Chapter 7: D/A and A/D Converters:

No.	Questions
1.	Explain D/A converter R-2R Ladder circuits.
2.	Explain D/A converter binary Weighted Resistor.
3.	Explain Counter type A/D Converter.
4.	Explain Successive Approximation A/D converter.
5.	Explain Dual slop type A/D converter.
6.	Explain the D/A converter Specifications.
7.	Explain the A/D converter Specifications.
8.	Explain Flash Type A/D converter.